

ATMega328 Microcontroller Project (Digital Temperature Meter)

Description:

Design a digital temperature meter system using ATmega328 microcontroller to read the temperature signal and display the reading in °C and °F using three seven segments.

Components required:

Component	Quantity	Notes
Breadboard	1	-
ATMega328P	1	Microcontroller
LM35	1	Temperature Sensor
330 or 510 Ohm	7	Resistor
10 KOhm	1	Resistor
7 Segment	3	Common Cathode
Push Buttons	3	2 Pins Button
Jumpers or wires	Around 40	High Quality Jumpers or telephone wires

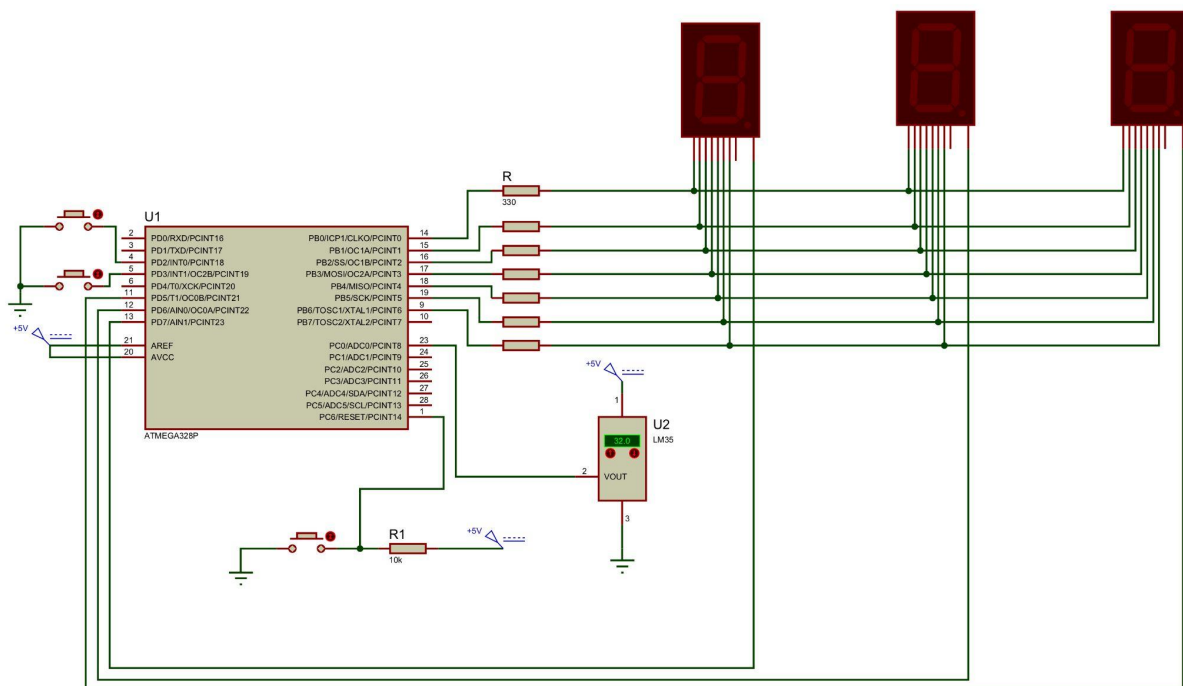


Figure [1]: Full schematic diagram of Digital Temperature Meter based on ATmega328P

ICs' Pin Configurations:

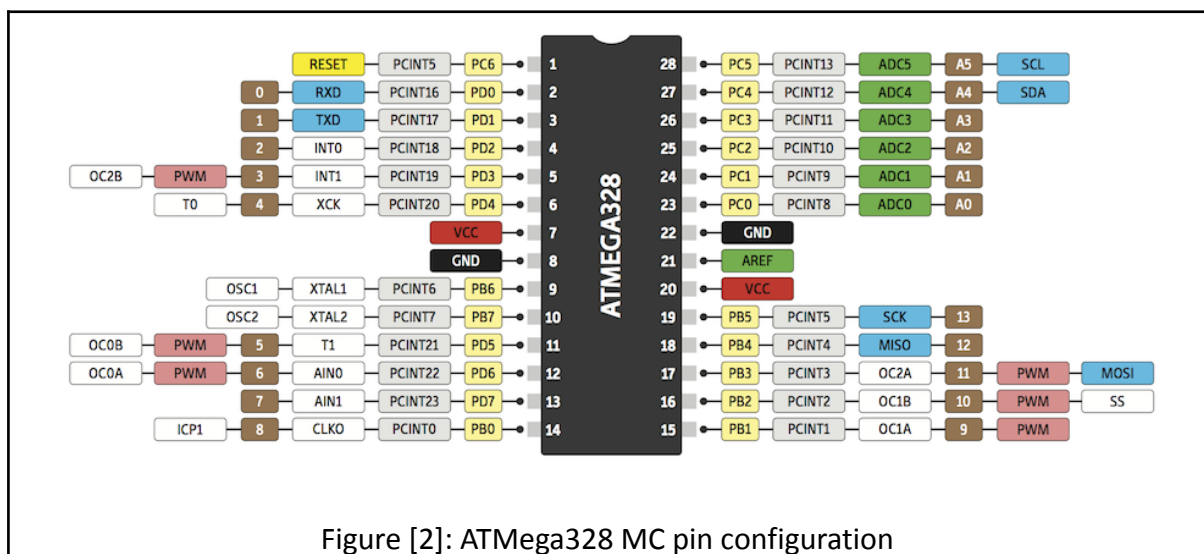


Figure [2]: ATmega328 MC pin configuration

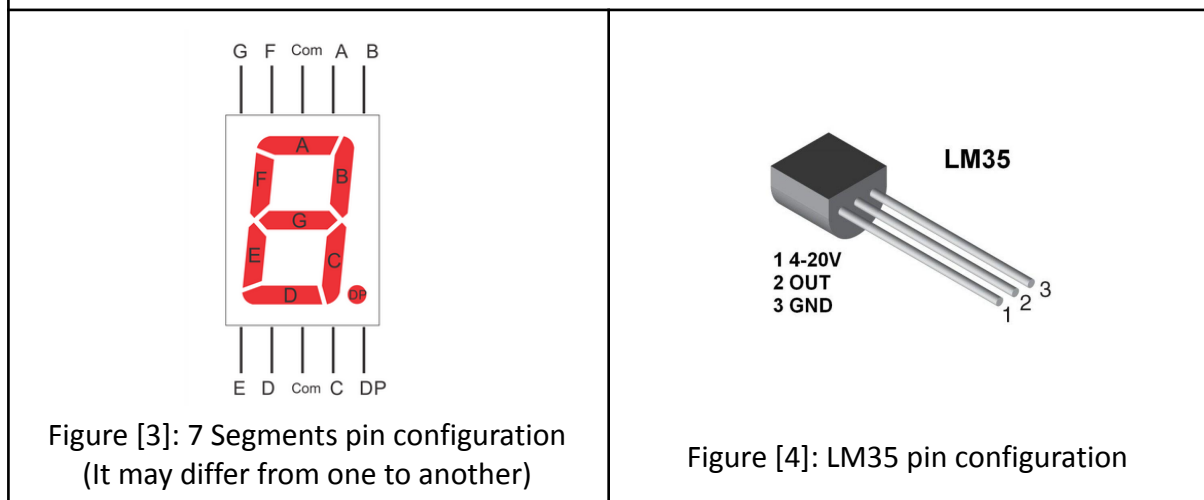


Figure [3]: 7 Segments pin configuration
(It may differ from one to another)

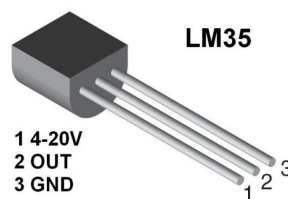


Figure [4]: LM35 pin configuration

Procedures:

- Construct the digital temperature meter circuit given in figure [1] on a test board.
- Write a C program using ATMEL Studio to perform the following tasks:
 - Convert analog signal (LM35 output) using ATmega328 internal ADC in free running mode.
 - Calculate temperature in $^{\circ}\text{C}$ and $^{\circ}\text{F}$ using the following equations:
 - Temp in $^{\circ}\text{C}$ = ADC Reading / 2.046
 - Temp in $^{\circ}\text{F}$ = (Temp in $^{\circ}\text{C} \times 9/5) + 32$
 - Use external interrupts INT0 and INT1 to switch between $^{\circ}\text{C}$ and $^{\circ}\text{F}$ modes.
 - Use timer0 in CTC mode to display the temperature on three 7 segments using time multiplexing technique.
- Build the Solution using the Build menu in ATMEL Studio to generate a .hex file.
- Use Extreme Burner Software to write the .hex file to the Microcontroller using your own programmer or Arduino board.